

数字系统设计

郑海永

上课时间地点：周 2/9 10 节/3308
电子信息科学与技术 2010 级和 2011 级

中国海洋大学 电子工程系

2013 年 4 月



VHDL

- ① 硬件描述语言
- ② VHDL 基础
- ③ **VHDL 实例**
- ④ VHDL 入门
- ⑤ VHDL 基本语句
- ⑥ VHDL 深入

目录

1 Examples


- 半加器
- 2选1多路选择器
- 2-4 解码器
- 1位全加器
- 高电平锁存的 n 位锁存器
- 上升沿触发的 D 触发器
- 时钟周期信号



半加器

半加器

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

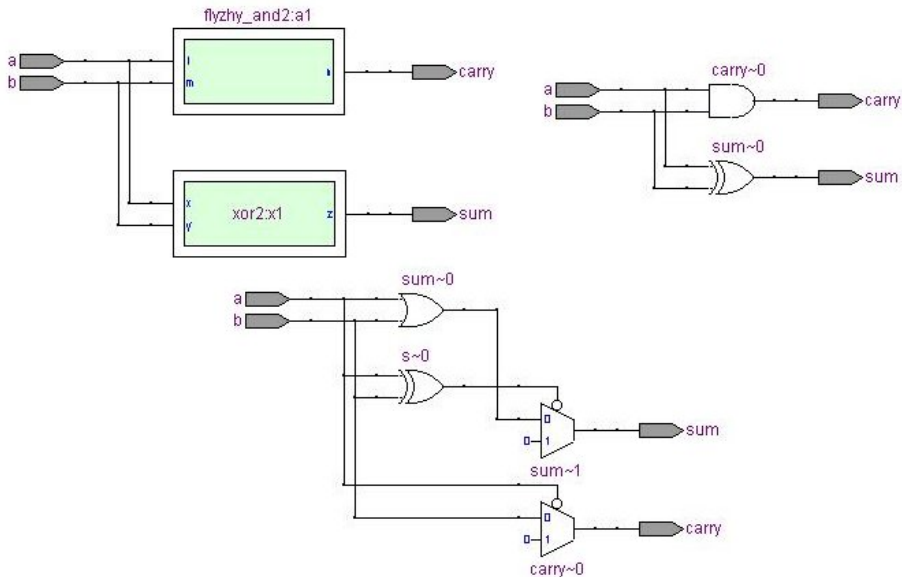



2选1多路选择器

2 选 1 多路选择器

$$out1 = \begin{cases} a & \text{if } c = 0, \\ b & \text{if } c = 1. \end{cases}$$

实体声明

```
1 ENTITY inverter IS
2   PORT(a: IN Bit; b: OUT Bit);
3 END inverter;
4 ARCHITECTURE inv_arch OF inverter IS
5 BEGIN
6   b <= NOT a;
7 END inv_arch;

9 ENTITY nand2 IS
10  PORT(a, b: IN Bit; c: OUT Bit);
11 END nand2;
12 ARCHITECTURE nand2_arch OF nand2 IS
13 BEGIN
14   c <= a NAND b;
15 END nand2_arch;

17 ENTITY mux IS
18  PORT(a, b, c: IN Bit; out1: OUT Bit);
19 END mux;
```


结构体—结构描述 \Leftrightarrow 逻辑图

```
1 ARCHITECTURE mux_arch1 OF mux IS
2   SIGNAL a_n, b_n, c_not: Bit;
3   COMPONENT inverter
4     PORT(a: IN Bit;
5           b: OUT Bit);
6   END COMPONENT;
7   COMPONENT nand2
8     PORT(a, b: IN Bit;
9           c: OUT Bit);
10  END COMPONENT;
```


```
1 BEGIN
2   U0: inverter PORT MAP(a => c, b => c_not);
3   U1: nand2 PORT MAP(a => a, b => c_not, c => a_n);
4   U2: nand2 PORT MAP(a => b, b => c, c => b_n);
5   U3: nand2 PORT MAP(a => a_n, b => b_n, c => out1);
6 END mux_arch1;
```

```
1 BEGIN
2   U0: inverter PORT MAP(c, c_not);
3   U1: nand2 PORT MAP(a, c_not, a_n);
4   U2: nand2 PORT MAP(b, c, b_n);
5   U3: nand2 PORT MAP(a_n, b_n, out1);
6 END mux_arch1;
```



结构体—行为描述 \Leftrightarrow 真值表 (状态图)

```
1 ARCHITECTURE mux_arch3 OF mux IS  
2 BEGIN  
3   PROCESS(a, b, c)  
4     BEGIN  
5       IF c='0' THEN  
6         out1 <= a;  
7       ELSE  
8         out1 <= b;  
9       END IF;  
10    END PROCESS;  
11 END mux_arch3;
```

2 选 1 多路选择器行为描述

 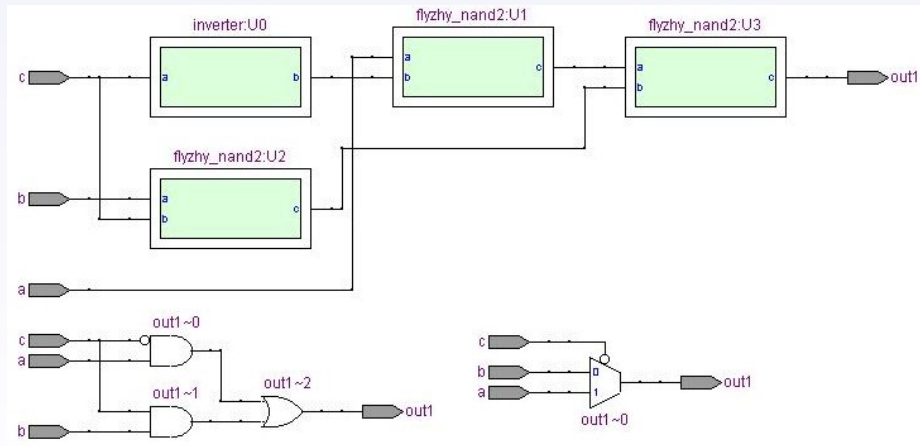

2 选 1 多路选择器



内容提要

1 Examples

- 半加器
- 2选1多路选择器
- 2-4 解码器
- 1位全加器
- 高电平锁存的 n 位锁存器
- 上升沿触发的 D 触发器
- 时钟周期信号

2-4 解码器

2-4 解码器

enable	a	b	z(0)	z(1)	z(2)	z(3)
0	x	x	1	1	1	1
1	0	0	0	1	1	1
	0	1	1	0	1	1
	1	0	1	1	0	1
	1	1	1	1	1	0


实体声明

```
1 ENTITY decoder2x4 IS
2   PORT(a, b, enable: IN Bit;
3         z: OUT Bit_Vector(0 TO 3));
4 END decoder2x4;
```


结构体—结构描述 \Leftrightarrow 逻辑图

```
1 ARCHITECTURE dec_str OF decoder2x4 IS
2   COMPONENT inv
3     PORT(pin: IN Bit; pout: OUT Bit);
4   END COMPONENT;
5   COMPONENT nand3
6     PORT(d0, d1, d2: IN Bit; dz: OUT Bit);
7   END COMPONENT;
8   SIGNAL abar, bbar: Bit;
9 BEGIN
10  v0: inv PORT MAP(a, abar);
11  v1: inv PORT MAP(b, bbar);
12  n0: nand3 PORT MAP(enable, abar, bbar, z(0));
13  n1: nand3 PORT MAP(abar, b, enable, z(1));
14  n2: nand3 PORT MAP(a, bbar, enable, z(2));
15  n3: nand3 PORT MAP(a, b, enable, z(3));
16 END dec_str;
```


2-4 解码器结构描述

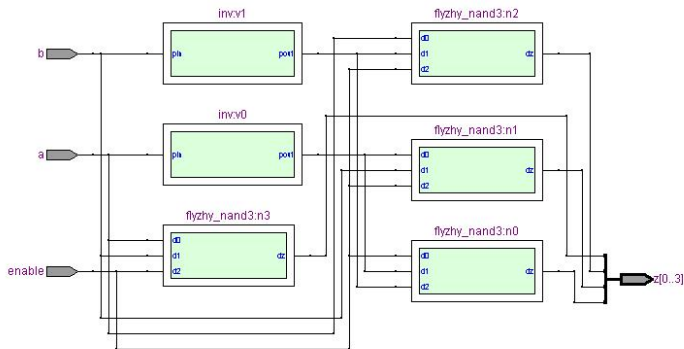

结构体—数据流描述 \Leftrightarrow 逻辑表达式 (布尔方程)

```
1 ARCHITECTURE dec_dataflow OF decoder2x4 IS
2   SIGNAL abar, bbar: Bit;
3 BEGIN
4   z(3) <= NOT (a AND b AND enable);
5   z(0) <= NOT (abar AND bbar AND enable);
6   bbar <= NOT b;
7   z(2) <= NOT (a AND bbar AND enable);
8   abar <= NOT a;
9   z(1) <= NOT (abar AND b AND enable);
10 END dec_dataflow;
```


2-4 解码器数据流描述

 

结构体—行为描述

```
1 ARCHITECTURE dec_sequential OF decoder2x4 IS
2 BEGIN
3     PROCESS(a, b, enable)
4         VARIABLE abar, bbar: Bit;
5         BEGIN
6             abar := NOT a;
7             bbar := NOT b;
8             IF enable = '1' THEN
9                 z(3) <= NOT (a AND b);
10                z(0) <= NOT (abar AND bbar);
11                z(2) <= NOT (a AND bbar);
12                z(1) <= NOT (abar AND b);
13            ELSE
14                z <= "1111";
15            END IF;
16        END PROCESS;
17    END dec_sequential;
```

2-4 解码器行为描述

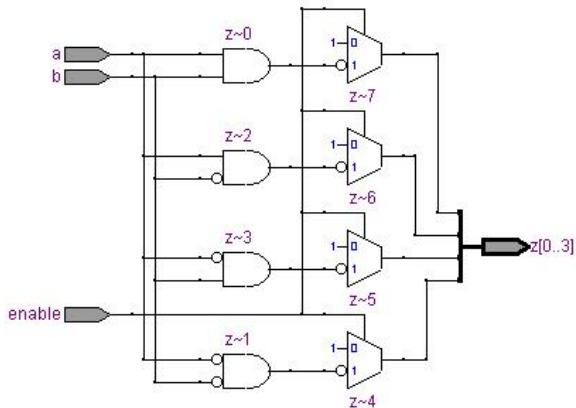

结构体—行为描述 \Leftrightarrow 真值表 (状态图)

```

1 ARCHITECTURE dec_sequential OF decoder2x4 IS
2 BEGIN
3   PROCESS(a, b, enable)
4     VARIABLE temp: Bit_Vector(1 DOWNTO 0);
5     BEGIN
6       temp := a & b;
7       IF enable = '1' THEN
8         CASE temp IS
9           WHEN "00" => z <= "0111";
10          WHEN "01" => z <= "1011";
11          WHEN "10" => z <= "1101";
12          WHEN "11" => z <= "1110";
13          WHEN OTHERS => z <= (OTHERS => '1');
14        END CASE;
15      ELSE
16        z <= (OTHERS => '1');
17      END IF;
18    END PROCESS;
19  END;
```

内容提要

1 Examples


- 半加器
- 2 选 1 多路选择器
- 2-4 解码器
- 1 位全加器
- 高电平锁存的 n 位锁存器
- 上升沿触发的 D 触发器
- 时钟周期信号

数据流描述 \Leftrightarrow 逻辑表达式 (布尔方程)

```
1 ENTITY full_adder IS
2   PORT(a, b, c_in: IN Bit;
3         sum, c_out: OUT Bit);
4 END full_adder;

6 ARCHITECTURE rtl OF full_adder IS
7   SIGNAL temp_sum: Bit;
8 BEGIN
9   temp_sum <= a XOR b AFTER 20 ns;
10  sum <= temp_sum XOR c_in AFTER 20 ns;
11  c_out <= (a AND b) OR (temp_sum AND c_in) AFTER 22 ns;
12 END rtl;
```

1 位全加器数据流描述

 

内容提要

1 Examples


- 半加器
- 2 选 1 多路选择器
- 2-4 解码器
- 1 位全加器
- 高电平锁存的 n 位锁存器
- 上升沿触发的 D 触发器
- 时钟周期信号

高电平锁存的 n 位锁存器

```
1 ENTITY latch IS
2   GENERIC (n: Positive := 8);
3   PORT (eg: IN Bit;
4         d: IN Bit_Vector(n-1 DOWNTO 0);
5         q: OUT Bit_Vector(n-1 DOWNTO 0));
6 END latch;

8 ARCHITECTURE latch_eg OF latch IS
9 BEGIN
10  PROCESS(eg)
11  BEGIN
12    IF eg='1' THEN
13      q <= d;
14    END IF;
15  END PROCESS;
16 END latch_eg;
```

高电平锁存的 n 位锁存器行为描述

 

内容提要

1 Examples

- 半加器
- 2选1多路选择器
- 2-4解码器
- 1位全加器
- 高电平锁存的n位锁存器
- 上升沿触发的D触发器
- 时钟周期信号

上升沿触发的 D 触发器


```

1 ENTITY dff IS
2     PORT (clk, d: IN Bit;
3           q, q_n: OUT Bit);
4 END dff;

6 ARCHITECTURE dff_bhv OF dff IS
7 BEGIN
8     PROCESS(clk)
9     BEGIN
10        IF clk'Event AND clk='1' THEN
11            q <= d;
12            q_n <= NOT d;
13        END IF;
14    END PROCESS;
15 END dff_bhv;

```

上升沿触发的 D 触发器行为描述

 

时钟周期信号

周期为 20ns 的时钟信号

```
1  clk <= NOT clk AFTER 10 ns;
```



不同开关时间的时钟波形

```
1  PROCESS
2  BEGIN
3    clk <= '0';
4    WAIT FOR 20 ns;
5    clk <= '1';
6    WAIT FOR 12 ns;
7  END PROCESS;
```

时钟周期信号

周期为 20ns 的时钟信号

```
1 clk <= NOT clk AFTER 10 ns;
```



不同开关时间的时钟波形

```
1 PROCESS
2 BEGIN
3   clk <= '0';
4   WAIT FOR 20 ns;
5   clk <= '1';
6   WAIT FOR 12 ns;
7 END PROCESS;
```

